

Carry bag & Envelope making, Bhoomithrasena training: 21 Feb 2019

F - 4683



- III. A) a) Explain with suitable diagrams the different modes of shift register operation.
b) Give the design of a ring counter and explain its operation.

OR

- III. B) a) What is race around condition? Explain the working of a Master-Slave JK flip-flop.
b) Give the design of a 3-bit binary counter using JK flip-flops.

15

- IV. A) a) Explain the operating mechanisms, characteristics and uses of strain gauge, LVDT, thermistors and thermocouples.
b) Distinguish between active and passive transducers.

OR

- ✓ IV. B) a) Discuss the various kinds of distortions and signal loss mechanisms encountered in fibre optic systems.
b) What are the advantages of PIN photodiode?

15

PART - C

Answer **any three** questions. Each question carries **five** marks.

- V. a) A power amplifier has a power gain of 40 dB. If an input power of 3 mW is applied then calculate the output power.
b) An opamp square wave oscillator is required to oscillate at a frequency of 2.5 kHz. Calculate the value of timing resistance if the value of timing capacitor used is $0.1 \mu\text{F}$. The feedback factor β is 0.5.
c) Design a 4-bit synchronous binary counter using J-K flip-flops and logic gates.
d) Design a 8-bit parity generator circuit.
e) A fibre optic cable is 20 km long. The measured ratio of input power to output power is 45. Calculate the attenuation of the fibre in dB per km.
f) A step index multimode optical fibre is having a core refractive index of 1.59 and cladding refractive index 1.47. Calculate the numerical aperture of the fibre. (3×5=15 Marks)

























